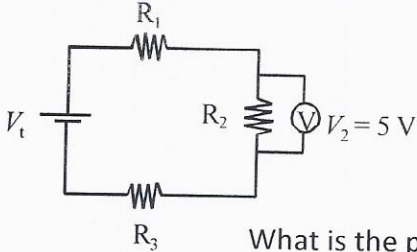


Enriched Circuit #2 Worksheet


1. The following electric circuit consists of a power source, three identical resistors (R_1 , R_2 and R_3) and a voltmeter V . The potential difference (voltage), V_2 , across R_2 is 5 V.



$$5 + 5 + 5 = 15 \text{ V}$$

What is the potential difference (voltage), V_t , across the terminals of the power source?

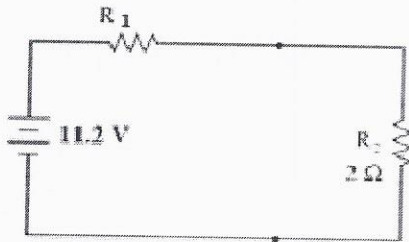
2. If the current intensity of the circuit is 0.035 A, what is the resistance for ' R_1 '?



$$R_T = \frac{V_T}{I_T} = \frac{11.2}{0.035} = 320 \Omega$$

$$320 - 2 = 318 \Omega$$

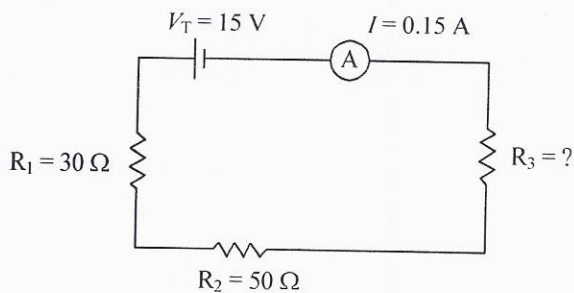3. The following electric circuit consists of a power supply, an ammeter A and three resistors (R_1 , R_2 and R_3). The voltage across the power supply is 15 V, and the ammeter reads 0.15 A.




$$R_T = \frac{V_T}{I_T} = \frac{15}{0.15} = 100 \Omega$$

$$100 \Omega - 80 \Omega = 20 \Omega$$

What is the value of R_3 ?

- A) 20 Ω
 B) 33 Ω
 C) 80 Ω
 D) 100 Ω

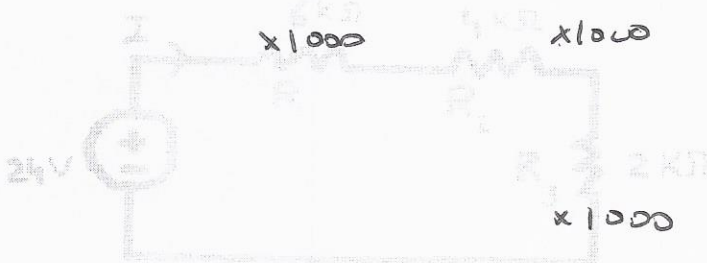
4. What is the current intensity of the circuit? To convert a $\text{k}\Omega$ to an Ω , multiply by 1 000.



$$I_T = \frac{V_T}{R_T} = \frac{24}{12000}$$

$$0.002 \text{ A}$$

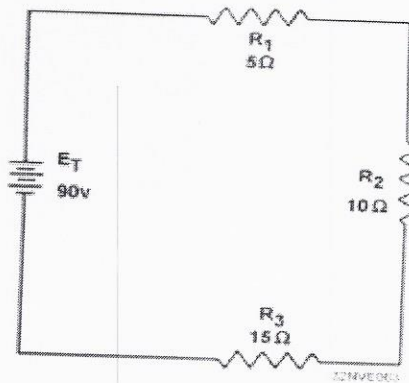
5. What is the potential difference for R_3 ?



$$V = RI \quad 15 \times 3 = 45 \text{ V}$$

$$I_T = \frac{V_T}{R_T} \quad \frac{90}{30} = 3 \text{ A}$$

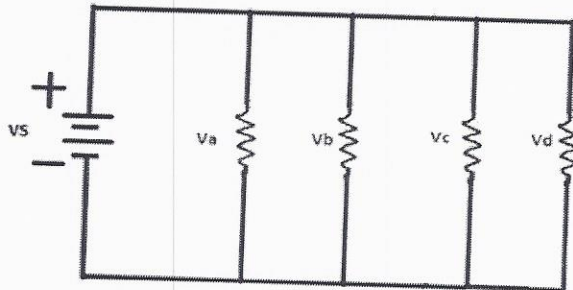
6. All resistors are of equal strength. The voltage for V_a is 25 V and the current going through V_a is 0.55 A. What is the equivalent resistance of the circuit?



$$R = \frac{V}{I} \quad \frac{25}{0.55} = 45.5 \Omega$$

$$\frac{1}{45.5} + \frac{1}{45.5} + \frac{1}{45.5} + \frac{1}{45.5} = 11.4 \Omega$$

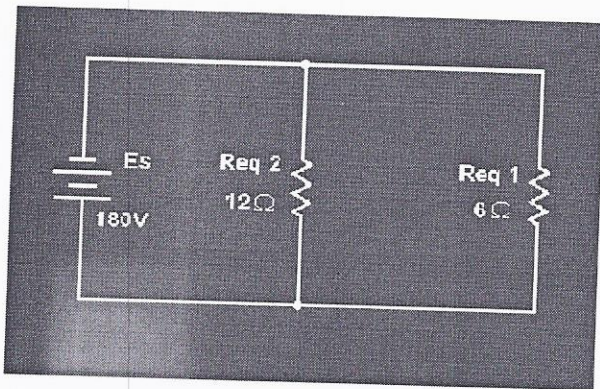
7. What is the current intensity coming from the power source?



$$I_T = \frac{V_T}{R_T} = \frac{180}{4 \Omega} = 45 \text{ A}$$

$$\frac{1}{12} + \frac{1}{6} = 4 \Omega$$

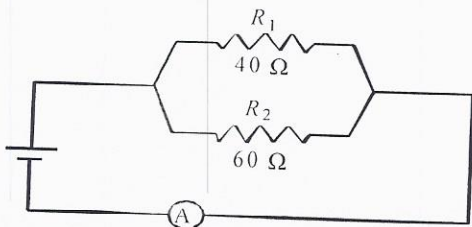8. The following circuit consists of a power supply, two resistors (R_1 and R_2) and an ammeter.




$$V = RI \quad 40 \times 2 = 80 \text{ V}$$

$$\frac{1}{40} + \frac{1}{60} = 24 \Omega$$

$$I_T = \frac{V_T}{R_T} \quad \frac{80}{24} = 3.3 \text{ A}$$

The current through resistor R_1 is 2 A. What is the current indicated by the ammeter?

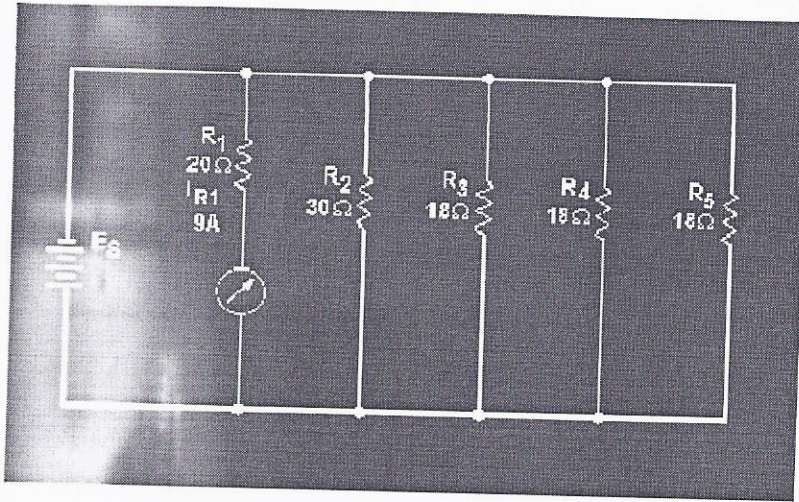9. What is the current intensity for R_3 and the current intensity from the power source?




$$V = R I$$

$$20 \times 9 = 180 \text{ V}$$

$$I_T = \frac{V_T}{R_T} = \frac{180}{4} = 45 \text{ A}$$


$$I_3 = \frac{V}{R} = \frac{180}{18} = 10 \text{ A}$$

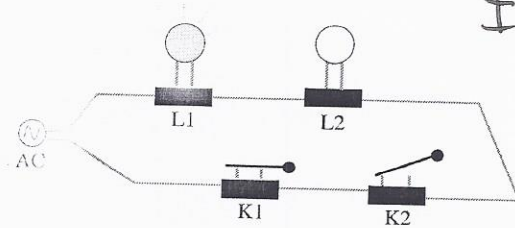10. What is wrong with the picture below?




In a series circuit, if the switch is open you cannot have a light on because there is no current.

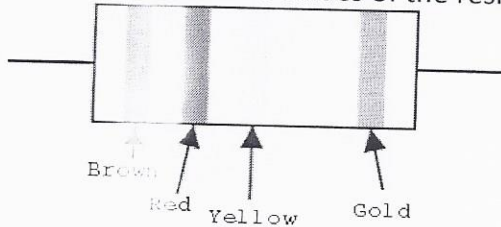11. What are the values of the resistors?



$$12 \times 10^4 \pm 5\%$$

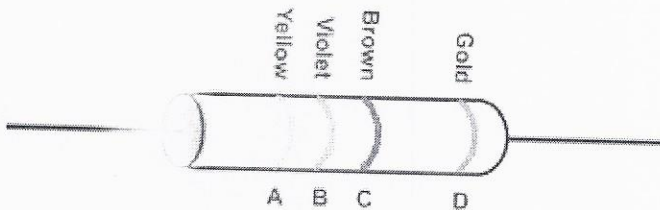

$$47 \times 10^1 \pm 5\%$$

12. Identify the colours associated with the resistors if they have the following resistances.

a) $23\,000 \Omega \pm 20\%$

red - orange - orange black

b) $44 \Omega \pm 10\%$

yellow - yellow - black silver




c) $180 \Omega \pm 5\%$

brown - grey brown - gold

13. Match the following terms with the pictures below:


- a) single pole-single throw
- b) single pole-double throw

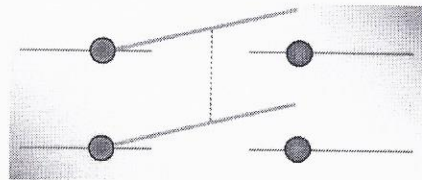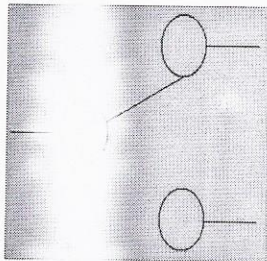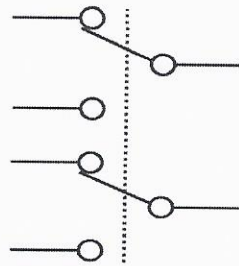- c) double pole-single throw
- d) double pole-double throw



14. Name the appropriate type of switch for the following functions:
- a) opening or closing two contacts at once and contact has one path **DPST**
 - b) opening one or the other of two circuits **DPDT**
 - c) opening one or the other of one circuit **SPST**

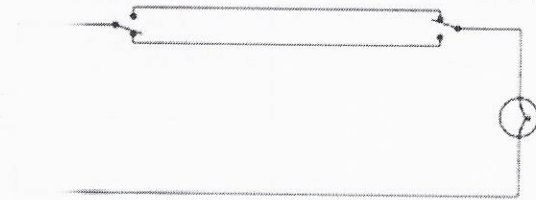
15. What positions do the switches have to be in for the light bulb to receive power?



both up or down
no current goes through

16. Consider the circuit diagram below.

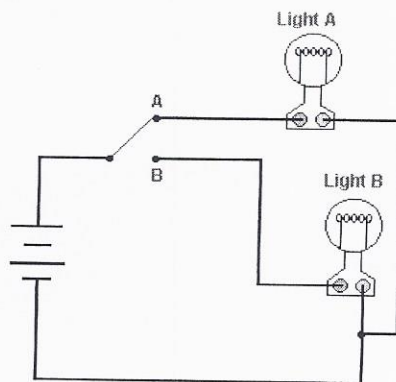- a) Name the switch. **SPDT**
- b) How must the switch be placed so that light bulb A comes on? **as is**
- c) Can light bulb A ever be on at the same time as light bulb B?




No, either A or B


17. Nicolas has decided to participate in the *Engineering Challenge*. This year he plans to build a racecar that can move around obstacles. He needs a resistor to slow down the motor. He asks the laboratory technician for a resistor offering a resistance between 8Ω and 12Ω . She offers him the four resistors below.

Which of the following resistors should Nicolas use?

Resistor 1 :

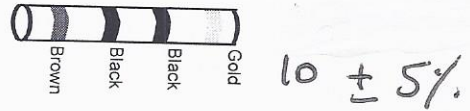

Resistor 2 :

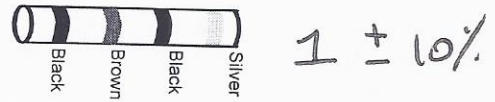



Resistor 3 :



Resistor 4 :



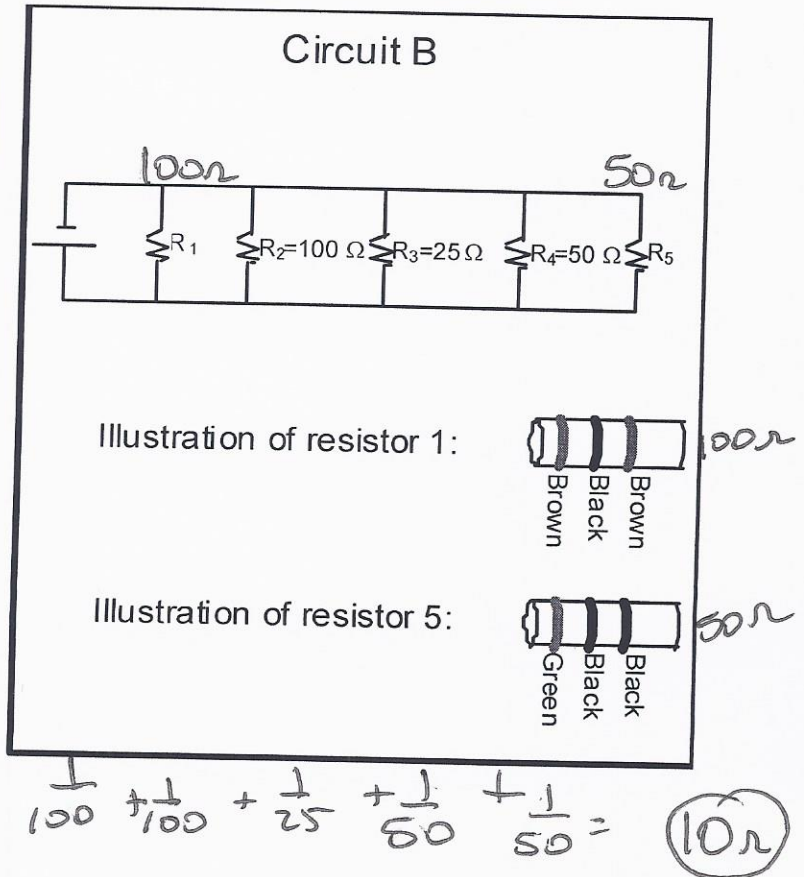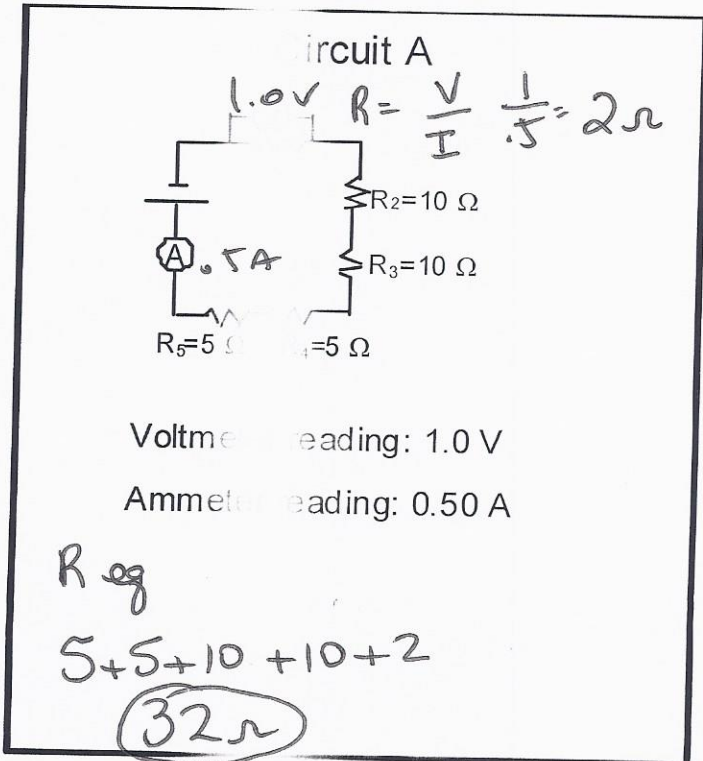18. Refer to the illustration of Circuit A and Circuit B in Figure 4 below. Which of the two circuits (Circuit A or Circuit B) has the greatest resistance?



↑ greatest resistance

19. Your friend wants to add some electrical accessories to the circuit of his automobile. The circuit must supply 4 pieces of equipment : a de-mister (M), a small pump (M) and 2 doorbells. Each item can function with a 6 V or a 12 V power supply.

The car's circuits provide a maximum of 12 volts.
He proposes two ways of connecting the equipment.

DIAGRAM A


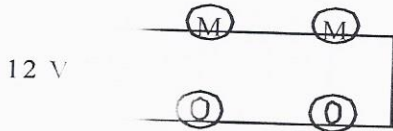



DIAGRAM B

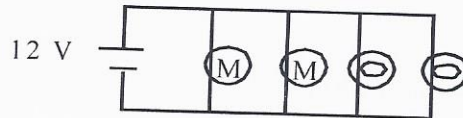

Which diagram must he choose for each item to function properly?
Justify your answer.

Diagram B - de-mister & pump each getting 6 or 12V, but voltage not added up. Diagram A all voltages would

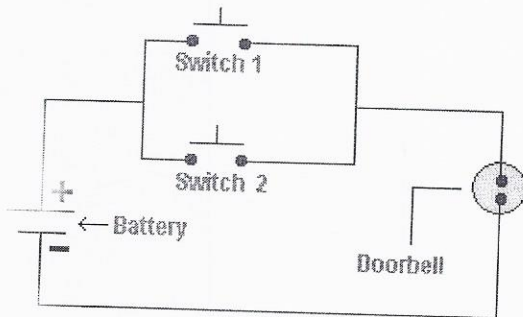20. Which switch must be closed for the doorbell to ring in the circuit below?



be added & would surpass 12V.

Either switch 1 or 2.